

---

**Important:** Do not draw the circuits by hand; instead, you should use the CircuitVerse simulation tool. <https://circuitverse.org/simulator> When you are done, export your file (Project → Export File). Name your file First-Name.LastName.HW2.cv and upload it to Gradescope. This will export a single file containing all three problems. Note: Save each problem as a different circuit.

---

**Collaboration Policy: For this homework only!** You may collaborate with other students in this class. As an **exception** to the usual collaboration policy, you do not need to tell us about casual interactions of the "I got X, what did you get?" variety. But **do** cite any close collaboration or major corrections; for example, if the answer to the above hypothetical was "I think X is wrong, here's why," and then you change your answer, add a note like "mst3k suggested this answer" next to your answer. However, we expect that everyone will work on the assignment to better understand circuits, so **you may not directly copy another student's answer.**

---

### PROBLEM 1 *4-bit Shifter.*

Design a circuit that accepts two inputs: a 4-bit number and a 2-bit wide input shift amount. The circuit's purpose is to generate a 4-bit output that reflects the input number after a bitwise left shift. Importantly, this circuit should operate without relying on a clock signal. Use ground for inputs that are zeros. Please label all your inputs and outputs.

### PROBLEM 2 *4-bit Increment.*

In class, we considered a counter circuit which counted from 0b000 to 0b111 and then back to 0b000. Design a counter circuit that "stops" at  $x = 0b1111$ . That is, if  $x$  is not all 1s, then increment by 1. If  $x$  is all 1s, then increment by 0, i.e.,  $z = 0b1111$ . Feel free to use the Full Adder component under Misc. Think about how you can turn a Full Adder into a half adder by setting inputs. Also, feel free to wire up the reset line on your flip flops to reset them for testing. Please label all your inputs and outputs.

### PROBLEM 3 *Register File.*

Create a register file comprising four register banks, each capable of storing 4 bits. The register file should have four input signals: a clock signal, a write enable line, a 2-bit wide register number selector, and a data line. Furthermore, the register file should feature a single 4-bit wide output, representing the value currently stored in the selected register. Please label all your inputs and outputs.